

ECE486 Final Project

by William Harrington

Introduction

The objective of this project was to design, model, simulate, and test an application specific-processor for cryptographic block cipher algorithms. The target algorithm was International Data Encryption Algorithm. However, the system should've been designed to achieve high throughput and low latency for executing block cipher algorithms in general, not just the IDEA algorithm.

Cyptographic block cipher algorithms

“A block cipher is a deterministic algorithm operating on fixed-length groups of bits, called blocks, with an unvarying transformation that is specified by a symmetric key”^[1]. Some example block ciphers are Data Encryption Standard, Advanced Encryption Standard, RC5, and Blowfish. Many block ciphers, including the ones just named, are ARX algorithms^[1], which means their operations only involve modular addition, bit rotation, and exclusive-or. Other simple logic operations and bit manipulations may also be involved.

Application-Specific Processor

This section explains in detail the application-specific processor that was designed to handle block cipher encryption algorithms.

Instruction Set Architecture (ISA)

The Instruction Set Architecture is the portion of the computer architecture that is visible to the programmer^[2]. This section discusses the analysis that was involved in choosing an ISA, and provides specification for the ISA that was chosen.

Analysis

The purpose of this analysis was to determine the best instruction set architecture for low latency. With regard to latency, memory latency is often a major concern. Since the processor was to be designed for block cipher algorithms which are typically ARX algorithms, a generic ARX algorithm was developed and used to analyze memory traffic with different instruction set architectures. The following were analyzed: Stack, Accumulator, Load-Store, and Memory-memory. The generic ARX algorithm is given below in traditional C syntax and then translated into assembly for each of the aforementioned architectures.

The following items were examined

- How many instruction bytes are fetched
- How many bytes of data are transferred from/to memory
- How much total memory traffic (code + data)

Generic ARX Algorithm in C syntax

The following assumptions are made for the code below

- A, B, C, D are unsigned 16-bit integers
 - They are initialized to some value and are in memory
- The function prototype for the rotate function is: `uint16_t Rotate(uint16_t toRotate, uint16_t amountOfRotation)`
 - The direction of the rotation makes no difference

```
Result = Rotate(A + B, C) ^ D;
```

Generic ARX Algorithm in assembly

The following assumptions are made for each instruction set

- The processor uses a 16-bit memory address and data operands
- The opcode is always one byte (8 bits).
- Memory accesses use direct, or absolute, addressing.
- The variables A, B, C, and D are initially in memory.
- For a load-store architecture, there are 16 general-purpose registers.
- When Mem[Addr] is used, this location in memory is NOT the same as A, B, C, D

Result is the place in memory where the result of the algorithm goes. Also, the mnemonics used are generic like those used in Computer Architecture, 5th edition by Hennessy and Patterson Appendix A Section 2.

Stack			Accumulator (Assume accumulator initialized to 0)		
-----			-----		
Push A	#&		Add A	#&	
Push B	#&		Add B	#&	
Add	#&		Store Mem[0]	%	
Pop Mem[0]	%		Rotate C	#&	
Push Mem[0]	#&		Store Mem[1]	%	
Push C	#&		XOR D	#&	
Rotate	#&		Store Result	%	
Pop Mem[1]	%				
Push Mem[1]	*#&				
Push D	#&				
XOR	#&				
Pop Result	%				
Load-Store			Memory-memory		
-----			-----		
Load R1, A	#&		Add Mem[0], A, B	#%	
Load R2, B	#&		Rotate Mem[1], C, Mem[0]	#%	
Add R3, R1, R2	#&		XOR Result, D, Mem[1]	#%	
Load R4, C	#&				
Rotate R5, R3, R4	#&				
Load R6, D	#&				
XOR R7, R5, R6	#&				
Store Result, R7	%				

* value is loaded from memory after having been loaded once

the result of one instruction is passed to another instruction as an operand

& storage within the processor

% storage in memory

Table 1: Comparison of memory traffic

Architecture	Instruction Bytes fetched	Bytes from/to mem	Code + Data
Stack	30	18	48
Accumulator	35	14	49
Load-store	32	10	42
Memory-memory	21	0	21

Conclusion and ISA choice

The memory-memory architecture had the least amount of total memory traffic. This means that memory latency is at a minimum and gives the optimal solution for latency. It also has the advantage of being most compact as it doesn't use extra registers for holding temporary variables like all the other architectures would.

There are downsides to this architecture however that are not apparent in the above analysis. For instance, there is a variation in instruction size when not using three-operand instructions. In the psuedo-code for the memory-memory architecture, three operands were used for each instruction. In the case of a two operand instruction, extra bits would have to be ignored somehow

or utilized in a different way. Also, the work per instruction would vary. As in the case of a two operand instruction like say Store or Load, the ALU isn't really needed. Lastly, memory accesses can create a bottleneck.

For the purpose of this project, throughput is most important which means having the least amount of total memory traffic is most desired. Therefore, the memory-memory ISA was chosen.

Instruction Format

Table 2: Instruction format

Opcode	Operand2	Operand1	Operand0
31-24	23-16	15-8	7-0

Table 4 shows the instruction format of the instruction set architecture. The numbers in the table represent the bit positions of each category. Thus the opcode is the MSB of the instruction while Operand0 is the LSB of the instruction. Operand2 is the 2nd MSB and Operand1 is the 2nd LSB. The length of the instruction is fixed. This was chosen because it emphasizes performance and reduces the complexity of decoding.

Operand2 is the address in memory where the result is to be stored. Operand1 is the address in memory that provides the value for the first operand to be supplied to the ALU. Operand0 is the address in memory that provides the value for the second operand to be supplied to the ALU.

Traditionally, the operands supplied to an ALU are referred to as A and B. Operand1 is the equivalent of A and Operand0 is the equivalent of B.

Addressing modes

Addressing modes define how a given instruction set architecture identify the operands of each instruction. No addressing modes are supported in this ISA. The reason for behind this choice had to do with the fact that addressing modes primarily benefit the programmer and that was not a goal of this project. Thus, all addresses given by an instruction point to a value in memory and not some other object such as a register.

Opcodes

The table below specifies the opcodes available in the architecture along with providing an example usage and description.

Table 3: Opcodes given in hexadecimal along with usage examples and explanations.

OP	Encoding	Usage	Ex (hex)	Description
ADD	0x0	ADD Mem[Z], Mem[Y], Mem[X]	00 02 01 00	Mem[Z] = Mem[X] + Mem[Y]
SUB	0x1	SUB Mem[Z], Mem[Y], Mem[X]	01 02 01 00	Mem[Z] = Mem[X] - Mem[Y]
MUL	0x2	MUL Mem[Z], Mem[Y], Mem[X]	02 02 01 00	Mem[Z] = Mem[X] * Mem[Y]
OR	0x3	OR Mem[Z], Mem[Y], Mem[X]	03 02 01 00	Mem[Z] = Mem[X] Mem[Y]
AND	0x4	AND Mem[Z], Mem[Y], Mem[X]	04 02 01 00	Mem[Z] = Mem[X] & Mem[Y]
XOR	0x5	XOR Mem[Z], Mem[Y], Mem[X]	05 02 01 00	Mem[Z] = Mem[X] ^ Mem[Y]
LOAD	0x6	LOAD Mem[Y], Imm Val or Mem[X]	06 1111 01	Mem[Y] = Value or Mem[X]
STORE	0x7	STORE Imm Val or Mem[X], Mem[Y]	07 1111 02	Mem[Y] = Value or Mem[X]
BZ	0x8	BZ Mem[Z], Mem[Y], Mem[X]	08 03 02 01	Branch if Mem[Y]=0 or Mem[X]=0. Next PC = Mem[Z].
BEQ	0x9	BEQ Mem[Z], Mem[Y], Mem[X]	09 03 02 01	Branch if Mem[Y] == Mem[X]. Next PC = Mem[Z].

OP	Encoding	Usage	Ex (hex)	Description
BP	0xA	BP Mem[Z], Mem[Y], Mem[X]	0A 03 02 01	Branch if Mem[Y] > 0 or Mem[X] > 0. Next PC = Mem[Z].
BN	0xB	BN Mem[Z], Mem[Y], Mem[X]	0B 03 02 01	Branch if Mem[Y] < 0 or Mem[X] < 0. Next PC = Mem[Z].
JMP	0xC	JR Value	0C 00 00 00	Jump to instruction specified by value. Next PC = Value. Extra bits are ignored.
HALT	0xD	HALT	0D 00 00 00	Halt execution.
NOP	0xE	NOP	0E 00 00 00	No op.
MODM	0xF	MODM Mem[Z], Mem[Y], Mem[X]	0F 03 02 01	Multiplication modulo $2^{16} + 1$. Mem[Z] = (Mem[Y]*Mem[X]) % ($2^{16} + 1$)

Microarchitecture

The microarchitecture of a processor refers to the way hardware is implemented for a given ISA. This section discusses what hardware was designed to implement the memory-memory architecture described in the previous sections.

Design considerations

Since the architecture is memory-memory and minimizing latency is a goal of the project, the latency of the memory employed was of utmost importance. The details of these modules are discussed in the following sections but their latency clearly dictates the clock period to be used for the implementation. The ALU is the second most important part of the architecture. The reason for this is that the ALU has to finish operating on the operands before anything can be done with them such as writing back to memory or determining the outcome of a branch. With regard to encryption, in algorithms like IDEA, the latency of the ALU is especially prominent because of sophisticated operations like multiplication modulo $2^{16} + 1$. These considerations played a major role in the development of the memory and ALU.

Overview

The components chosen for the microarchitecture were:

- Program Counter
- Instruction Memory
- Instruction Register/Decoder
- Memory module
- Arithmetic Logic Unit (ALU)

These components were used to construct a 5-stage unpipelined multi-cycle processor. This means that it takes multiple cycles for an instruction to complete. Figure 1 depicts the organization of these components. The reason for this design choice had to do with the unrealistic constraints that a single-cycle processor would put on the memory and ALU. The architecture was not pipelined to eliminate the hardware overhead associated with hazards. Thus, these components compose a minimal solution for the ISA while still being able to handle the task of encryption.

Stages

Instruction Fetch

During this stage, the PC is incremented with its own internal adder. This takes one cycle to complete. Once complete the PC outputs a 16-bit integer that is address of the next instruction to grab from the instruction memory. The memory location specified by the output of the program counter is then accessed. The output of the instruction memory is a 32-bit instruction that is connected to the input of the instruction register/decoder.

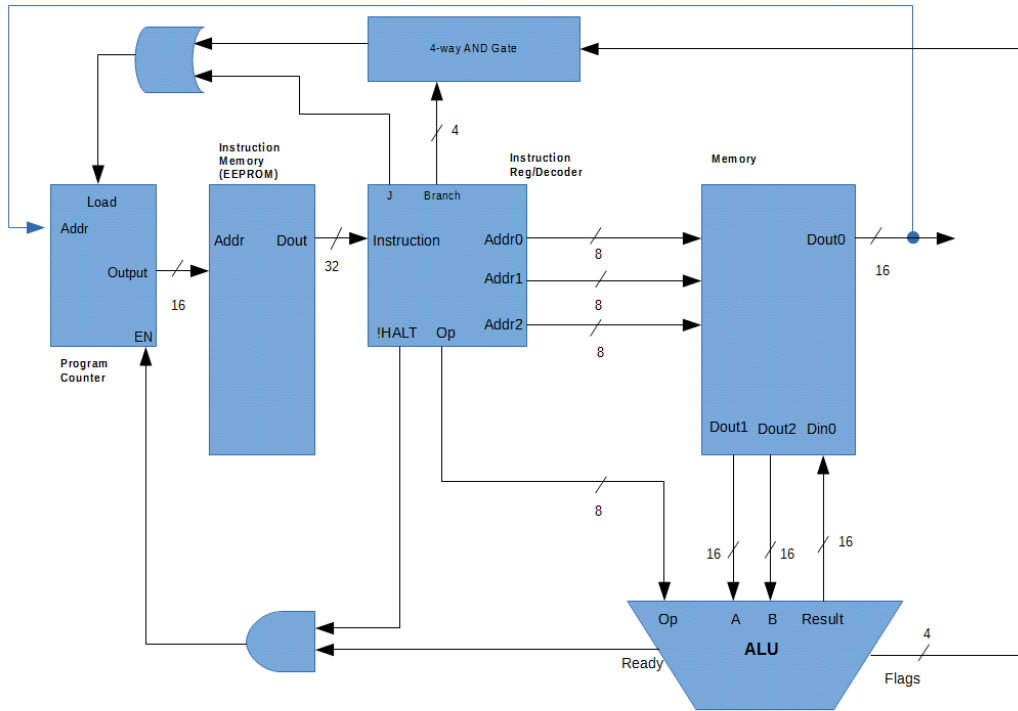


Figure 1: Application-Specific Processor Microarchitecture

Decode

The instruction is split up according to the instruction format specified by the ISA. The decoder looks for branch and jump instructions and sets the flags listed below.

- J - Jump
- Branch - Condition for branching
 - bz - branch if ALU zero flag is set
 - bn - branch if ALU negative flag is set
 - beq - branch if ALU equal flag is set
 - bp - branch if ALU positive flag is set

The branch flags are sent to a four way AND gate where they are ANDed with the flags from the ALU. The result of this ANDing is sent to an OR-gate where they are Ored with the jump flag. The result from the OR-gate is a control signal for the program counter. This control signal is an important part of branch completion.

As specified by the ISA, the instruction contains addresses for the operands to be sent to the ALU and the address of where the result should be stored in memory. These addresses are passed on to the memory module. The instruction also contains the op code which is passed on to the ALU. This stage takes one clock cycle to complete.

Memory Access

The memory module uses the addresses supplied by the decode stage to access those locations in memory and then pass them on to the ALU. This stage takes two cycles to complete.

Execute

The ALU uses the op code from the decode stage to determine what operation to perform once the memory module has supplied the operands. Once they are supplied, the ALU performs the operation and yields the result. The amount of cycle this stage takes to complete varies based on the operation to be performed.

Write Back / Branch Completion

Once the ALU has completed its operation, the result is written back to memory. At the completion of the operation the flags of the ALU are set. These flags are set regardless of the instruction being a branch. If the instruction is a branch, then they are used for determining the outcome of the branch.

Functional Description

Program Counter

The program counter outputs a 16-bit value that is the address of the next instruction within the instruction memory. The program counter is incremented only when the enable signal (EN) is asserted. This input is controlled by the logical AND'ing of the ALU ready signal and the !HALT signal from the IR/Decoder. Each time that EN is asserted the output of the PC increments to start the processing of the next instruction. The PC has another control signal called load. This signal causes the value on the address bus (Addr) to get latched into the PC and it becomes the next instruction that is fetched from the instruction memory. The load signal is controlled by the logical OR'ing of the jump signal (J) and the AND'ing of the branch bits (Branch) with the flag bits (Flags) from the ALU. The address bus (Addr) is driven by one of the address outputs of the IR/Decoder (Addr0). The PC has its own internal adder implemented with a ripple carry adder for incrementing and a register to hold its current value. The propagation delay of the adder is assumed to be less than half of the memory latency so that it only takes 1 clock cycle to increment.

Signals

- Inputs
 - Addr - 16 bit value used for jumping and breaks
 - * Connected Addr0 output of Instruction Register/Decoder
 - * Becomes next PC output when Load and En asserted
 - Load - Digital control signal used for jumping and breaks
 - * Connected to OR-gate output of branch and jump flags
 - En - Digital control signal used for incrementing the counter
 - * Connected to the AND-gate output of the ready signal from the ALU and !HALT from Instruction Register/Decoder
- Outputs
 - Output - 16 bit value that is the address of the next instruction to execute

Instruction Memory

The instruction memory contains the instructions to be executed. It was implemented with assumption of a modified PC100 SDRAM with the following timing parameters^{[3][4]}.

Data Rate	Bit time	Command Rate	Cycle Time
100 MT/s	10 ns	100 MHz	20 ns

Therefore, a clock frequency of 100 MHz was used for the processor. This memory is read-only and it takes 2 clock cycles to read from.

Signals

- Inputs
 - Addr - address of memory to access
 - * Connected to output of PC
 - * 16 bits wide
- Outputs
 - Dout - Data of memory address * Connected to input of IR/Decoder * 32 bits wide

Instruction Register/Decoder (IR/Decoder)

The instruction register/decoder separates the instruction into the pieces specified by the ISA and passes these pieces on to the memory module and ALU. It receives a 32-bit instruction from the instruction memory and parses the most significant

8-bits, which represent the opcode, to detect what kind of operation is getting ready to happen. If a halt is detected, it drives the !HALT signal low, causing the PC to stop incrementing. If a jump is detected, it drives the J signal high which asserts the load signal on the program counter. The branch bits (Branch) are passed on to a 4-way AND gate where they are AND'd with the flag bits (Flags) from the ALU. The op bits are then passed on to the ALU. The 24 bits after the op code are separated into three 8-bit addresses that are passed on to the memory module.

Signals

- Inputs
 - Instruction - 32 bit instruction
 - * Connected to output of instruction memory
- Outputs
 - J - jump flag
 - * Connected to OR gate with result of 4-way AND gate of branch bits
 - Branch - Branch bits
 - * bz - branch zero instruction detected
 - * bn - branch negative instruction detected
 - * beq - branch eq instruction detected
 - * bp - branch positive instruction detected
 - Connected to 4-way AND gate with flags from ALU
 - Addr0, Addr1, Addr2 - 8 bit addresses for memory access
 - * Connected to input of memory module
 - !Halt - Halt instruction detected, active low
 - * Connected to AND gate with ALU ready signal
 - Op - 8 bit op code
 - * Connected to ALU

Memory module

The memory module is a small quick memory that has 2 read only ports and 1 bi-directional port for reading and writing data. The bi-directional port is Port 0. This port is utilized by Operand0 which is the address in memory where the value is stored or the value in memory where the PC will jump/branch to. Port 1 and Port 2 are the ports for operands A and B respectively. These ports are read only. This design choice was made to help avoid memory bottlenecks and data hazards.

The memory module was implemented with assumption of a modified PC100 SDRAM with the following timing parameters^{[3][4]}.

Data Rate	Bit time	Command Rate	Cycle Time
100 MT/s	10 ns	100 MHz	20 ns

Therefore, a clock frequency of 100 MHz was used for the processor. It takes 2 clock cycles to read or write to the memory module.

Signals

- Inputs
 - Addr0, Addr1, Addr2 - Addresses to access
 - * Connected to outputs of IR/Decoder
 - * 8 bits wide
 - Din0 - Data input for Port 0
 - * Connected to output for ALU
 - * 16 bits wide
 - WE - Write enable for Port 0 (not pictured in diagram)
 - * Connected to ready signal on ALU
- Outputs
 - Dout1, Dout2 - Output value at addresses Addr1, Addr2
 - * Connected to A, B inputs of ALU
 - * 16 bits wide
 - Dout0 - Output value at address Addr0

- * Connected to Addr input of PC, used for branching/jumping
- * 16 bits wide

Arithmetic Logic Unit (ALU)

The ALU is a combinational circuits that performs arithmetic operations. This component is a crucial component of any processor. Special considerations were given to the ALU for this specific application. In particular, the ALU has to perform the multiplication modulo $2^{16} + 1$ as specified by the ISA. With a circuit like a ripple carry adder/subtractor, performing this operation would take a really long time thereby significantly reducing throughput. Instead of something archaic like the ripple carry adder, a bit-serial implementation^[5] was used to significantly reduce the clock cycles needed for this. This choice also allows the ALU to handle other operations quickly as well. It takes 35 clock cycles for a multiplication modulo operation and 1 for all other instructions specified by the ISA.

Signals

- Inputs
 - Op - 8 bit op code from instruction register/decode
 - A, B - 16 bit operands from memory
- Outputs
 - Result - 16 bit result for operation
 - * Connected to memory for write back
 - Flags - Flags for conditional branching
 - * N - One or both operands negative
 - * P - One or both operands positive
 - * Z - One or both operands zero
 - * E - Operands equal
 - Connected to 4-way AND gate whose output controls load on PC
 - Ready - Control signal connected to AND gate with !HALT from IR/Decoder

Instruction timing

Table 6: Instruction timing

OP	Clock cycles	OP	Clock cycles	OP	Clock cycles	OP	Clock cycles	OP	Clock cycles
ADD	9	STORE	9	BP	9	NOP	9	OR	9
SUB	9	MUL	9	BN	9	HALT	9	AND	9
BEQ	9	BZ	9	JR	9	MODM	43	XOR	9
LOAD	9								

Average clock cycles per instruction = 11.13

Throughput = 16 bits / (11.13*10ns) = 143.8 MBits/s

Design optimizations

Avoiding hazards

A Harvard architecture was chosen for instruction memory and data. This means that the instruction memory and data memory are separated. The program counter has its own internal also has its own internal ALU for addition. This means that the program counter doesn't need the ALU that performs operations on the operands to increment. These choices were made to avoid structural hazards.

Dealing with the memory bottleneck

The memory module has three ports with two being read-only. This means only one port can be written to. This choice was made to avoid a memory bottleneck.

Lowering latency

Since the architecture is memory-memory, small quick memories were used for the implementation of the instruction memory and memory module. This was done to minimize memory latency.

Maximizing throughput

The ALU uses a bit-serial implementation to quickly process sophisticated operations like multiplication modulo $2^{16} + 1$. A bit-serial implementation can handle multiplication modulo $2^{16} + 1$ in 35 clock cycles and all other operations specified by the ISA in 1 clock cycle.

International Data Encryption Algorithm

The International Data Encryption Algorithm (IDEA) is a symmetric-key block cipher that operates on 64-bit plaintext blocks. The encryption key is 128-bits long, and the same algorithm is used for both encryption and decryption. IDEA uses Exclusive-OR (\oplus), addition modulo 2^{16} (\boxplus), and multiplication modulo $2^{16} + 1$ (\odot) operations during its “rounds” for encryption and decryption. All operations are performed on 16-bit sub-blocks with a 16-bit subkey.

Key scheduling

IDEA uses 52 subkeys: six for each of the eight rounds and four more for the output transformation. In order to do this, the original key is broken up into six subkeys then rotated left by 25 bits. This is done until all 52 subkeys are created.

Algorithm for Encryption

The encryption and decryption algorithm is composed of 8 “rounds” that take 14 identical steps followed by a final output transformation that is referred to as a “half-round”. The operations are performed with a 64-bit plaintext block and a 128-bit key. The plaintext block is separated into four 16-bit sub-blocks: X_1, X_2, X_3, X_4 . The key is eventually broken down into 52 sub-keys. However, it is first split up into eight 16-bit sub-keys: K_1, \dots, K_8 . The first six (K_1, \dots, K_6) are used in the first round and the last two (K_7, K_8) are the first two used in the second round. The key is then rotated 25 bits to the left and split up into eight more 16-bit sub-keys: K_9, \dots, K_{16} . The first four (K_9, \dots, K_{12}) are used in round two after K_7, K_8 ; the last four are used in round 3. The key is rotated to the left again 25-bits to obtain the next eight subkeys, and so on until the end of the algorithm.^[6]

Table 7 lists the steps for each round and the equivalent assembly instruction for the architecture developed to show how it can be used to perform IDEA encryption.

Table 7: IDEA algorithm steps and their associated operation

Step	Operation	Instruction	Step	Operation	Instruction
1.	$X_1 \odot K_1$	MODM Mem[S_1], Mem[X_1], Mem[K_1]	8.	Step6 \boxplus Step7	ADD Mem[S_8], Mem[S_6], Mem[S_7]
2.	$X_2 \boxplus K_2$	ADD Mem[S_2], Mem[X_2], Mem[K_2]	9.	Step8 $\odot K_6$	MODM Mem[S_9], Mem[S_8], Mem[K_6]
3.	$X_3 \boxplus K_3$	ADD Mem[S_3], Mem[X_3], Mem[K_3]	10.	Step7 \boxplus Step9	ADD Mem[S_{10}], Mem[S_7], Mem[S_9]
4.	$X_4 \odot K_4$	MODM Mem[S_4], Mem[X_4], Mem[K_4]	11.	Step1 \oplus Step9	XOR Mem[S_{11}], Mem[S_1], Mem[S_9]
5.	Step1 \oplus Step3	XOR Mem[S_5], Mem[S_1], Mem[S_3]	12.	Step3 \oplus Step9	XOR Mem[S_{12}], Mem[S_3], Mem[S_9]
6.	Step2 \oplus Step4	XOR Mem[S_6], Mem[S_2], Mem[S_4]	13.	Step2 \oplus Step10	XOR Mem[S_{13}], Mem[S_2], Mem[S_{10}]

Step	Operation	Instruction	Step	Operation	Instruction
7.	$\text{Step5} \odot K_5$	MODM Mem[S_7], Mem[S_5], Mem[K_5]	14.	$\text{Step4} \oplus \text{Step10}$	XOR Mem[S_{14}], Mem[S_4], Mem[S_{10}]

The output of the round is the four sub-blocks: O_1, O_2, O_3, O_4 that are the results of steps 11, 12, 13, and 14. These are the input to the next round. This happens eight times and on the eight round the inner blocks are swapped then followed by a final output transformation.

The final output transformation consists of the four steps in the table below.

Table 8: The “half-round” transformation to finish IDEA encryption

Step	Operation	Instruction	Step	Operation	Instruction
1.	$X_1 \odot K_1$	MODM Mem[S_1], Mem[X_1], Mem[K_1]	3.	$X_3 \boxplus K_3$	ADD Mem[S_3], Mem[X_3], Mem[K_3]
2.	$X_2 \boxplus K_2$	ADD Mem[S_2], Mem[X_2], Mem[K_2]	4.	$X_4 \odot K_4$	MODM Mem[S_4], Mem[X_4], Mem[K_4]

These four steps are then combined to produce the 64-bit ciphertext.

Simulation

The architecture was simulated using python. The subkeys are pre-computed with the procedure described in the previous section. Memory image is initialized with the subkeys followed by the 1024 bits of plaintext. The key used was 0x7802c45144634a43fa10a15c405a4a42. The 1024 bits of plaintext were varied for testing purposes. However, for verification purposes, one block of plaintext was hardcoded to ensure the IDEA algorithm was working properly. This block of plaintext was 0x20822C1109510840.

The code for generating the memory image is in gtv.py and the algorithm for generating the subkeys is in IDEA.py. See generate_memory_image in gtv.py and create_subkeys in IDEA.py

The implementation of the IDEA algorithm for this architecture is in program.hex. The simulation showed that the program takes 40480 clock cycles to execute. With a clock period of 10ns, that is 404.8 microseconds. There is a README included with this report that explains how to run the simulation.

References

1. “Block Cipher” Wikipedia: The Free Encyclopedia. Wikimedia Foundation, Inc. 4 May 2016. Web. 2 June 2016.
2. Hennessy, John L., and David A. Patterson. Computer architecture: a quantitative approach (5th Edition). Elsevier, 2012.
3. “CAS Latency: Memory Timing Examples” Wikipedia: The Free Encyclopedia. Wikimedia Foundation, Inc. 2 June 2016. Web. 2 June 2016.
4. “PC100” Wikipedia: The Free Encyclopedia. Wikimedia Foundation, Inc. 10 March 2016. Web. 4 June 2016.
5. Leong, Monk-Ping, et al. “A bit-serial implementation of the international data encryption algorithm IDEA.” Field-Programmable Custom Computing Machines, 2000 IEEE Symposium on. IEEE, 2000.
6. Schneier, Bruce. Applied cryptography: protocols, algorithms, and source code in C. John Wiley & sons, 1996.